



Dynamic Behavior of Electronic Systems: R, L, and C

Dr. M. Kiran Kumar, K.Sai Sruthi, G.Sumalatha

Department of Electrical and communication Engineering, Anurag University, Ghatkesar, Telangana, India

ABSTRACT

In the context of electrical circuits, the essential components are resistance, inductance, capacitance play key role in shaping the behavior of electronic systems. Existing literature highlights that resistance impedes current flow, quantified by ohm's Law, while inductance stores energy in a magnetic field, following Faraday's Law. Capacitance stores charge in an electric field, governed by Coulomb's Law. Understanding resistance inductance and capacitance is vital for optimizing electric circuits, ensuring efficient energy transfer and signal transmission. This paper aims to provide insights into novel methods for calculating and managing these parameters, potentially filling gaps and advancing the current understanding in the field of electrical engineering. Resistance experimental setup involves using ohmmeter or multimeter to measure direct resistance in circuits. Inductance is often measured using inductance meters or calculated through experiments involving magnetic fields and changing currents. Capacitance is determined using capacitance meters or through experiments assessing charge and voltage relationship. The calculated or measured values for resistance, inductance, capacitance reveal intricate relationships within the electrical circuits. Patterns and trends emerge, illustrating how changes in one parameter impact the others, providing insights into the dynamic behavior of electronic systems. The findings bear practical significance by guiding the design of electric circuits for enhanced efficiency and reliability, This paper advances the understanding of Electrical properties of electronic components, offering insights that can inform optimized circuit configurations.

KEYWORDS:

Resistance(R), Inductance(L), Capacitance(C), capacitive reactance(X_c), inductive reactance(X_L), frequency(f).

I.INTRODUCTION

In the realm of electrical engineering and electronics, three fundamental properties are crucial for understanding the behavior of circuits and devices: resistance, capacitance, and inductance. These properties are inherent to different types of electrical components and play essential roles in the functioning of electronic systems. Resistance is a measure of how much a component or material opposes the flow of electric current. It is denoted by the symbol 'R' and measured in ohms (Ω). Resistors are passive electrical components designed specifically to introduce resistance into a circuit. Resistors dissipate electrical energy in the form of heat when current flows through them.

Capacitance refers to the ability of a system to store electrical charge. It is denoted by the symbol 'C' and measured in farads (F), although microfarads (μF) and picofarads (pF) are more commonly used in practical applications. Capacitors are passive components used to store and release electrical energy. They consist of two conductive plates separated by an insulating material (dielectric). Capacitors can store energy in an electric field when voltage is applied across them, and they release this stored energy when the voltage is removed. Inductance is the property of a circuit element (inductor) that opposes any change in the current flowing through it. It is denoted by the symbol 'L' and measured in henrys (H), although millihenry's (mH) and micro henrys (μH) are more common in practical applications. Inductors are passive components typically made of coils of wire. When current flows through an inductor, it generates a magnetic field around it. Any change in current induces a voltage in the inductor, opposing the change, according to Faraday's law of electromagnetic induction. Inductors store energy in a magnetic field when current flows through them and release this stored energy when the current changes. These three fundamental properties are interrelated and form the basis of many electrical circuits and systems. Understanding how resistance, capacitance, and inductance interact is essential for designing, analyzing, and

troubleshooting electronic circuits and devices. They are the building blocks upon which much of modern electronics is built.

II.METHODOLOGY

Resistance, capacitance, and inductance find wide-ranging applications across various fields due to their fundamental roles in electrical engineering. Resistors are used in voltage divider circuits to produce a fraction of the input voltage at the output. This is useful in applications like volume control in audio equipment. Resistors are often used to limit current flow in circuits, protecting components from excessive current. Thermistors, which are temperature-sensitive resistors, are used in temperature sensing applications such as thermostats and temperature-compensated circuits. Resistors are used in series with LEDs to limit the current flowing through them and prevent damage. Capacitors store electrical energy and are used in various applications such as power supply filtering, energy storage in flashlights and camera flashes, and smoothing voltage fluctuations in electronic circuits. Capacitors in conjunction with resistors are used to create timing circuits in applications like oscillators, timers, and pulse generators. Capacitors are used to couple signals between different stages of an amplifier while blocking DC, and they are also used for decoupling to stabilize the power supply voltage. Capacitors are used in filter circuits to remove unwanted frequency components from signals, such as in low-pass, high-pass, band-pass, and band-reject filters. Inductors generate magnetic fields when current flows through them, making them useful in applications such as electromagnets, magnetic sensors, and transformers. Inductors are used in filter circuits, especially in conjunction with capacitors, to remove unwanted frequency components from signals. Inductors are used in radio frequency (RF) circuits for tuning and filtering signals in applications such as radio receivers, transmitters, and wireless communication systems. Inductors are essential components in power supply circuits, DC-DC converters, and voltage regulators for energy storage and voltage regulation.

To measure resistance (R), instruments such as ohmmeters or multimeters are utilized. These devices apply a known voltage across the component under test and measure the resulting current, facilitating the calculation of resistance using Ohm's Law ($R = V/I$). Direct resistance measurements are often conducted in circuits using these instruments, aiding engineers in identifying faulty resistors during troubleshooting. Capacitance (C) is commonly measured using specialized capacitance meters. These meters apply a known voltage or current to the capacitor and measure the resulting charge or voltage, allowing for the determination of capacitance. Alternatively, experimental methods involve establishing the relationship between charge and voltage across the capacitor. By varying the applied voltage and measuring the resulting charge, capacitance can be accurately determined.

Inductance (L) is typically measured using inductance meters, which apply an alternating current (AC) to the inductor and measure the resulting magnetic flux or current. This facilitates the calculation of inductance. Experimental approaches involve assessing the behavior of inductors in magnetic fields with changing currents. For instance, by varying the current passing through an inductor and measuring the induced voltage, its inductance can be determined.

Resistance is a measure of the opposition to the flow of electric current through a conductor.

It is calculated using the formula:

$$R = \rho \cdot l / A$$

R = Resistance
 ρ = Resistivity of the material

l = Length of the conductor

A = Cross-sectional area of the conductor

Inductance is the property of an electrical conductor by which a change in current flowing through it induces an electromotive force (EMF) in both the conductor itself and in any nearby conductors.

It is calculated using the formula:

$$L = \mu_0 \mu_r N^2 A / l$$

L = Inductance

X_L = Inductive reactance f = Frequency of the alternating current

π = approximately 3.14

Capacitance is the ability of a system to store an electric charge.

It is calculated using the formula:

$$C = \epsilon_0 \cdot A / d$$

C = Capacitance

ϵ_0 = Permittivity of the material (e.g., vacuum permittivity)

A = Area of the plates of the capacitor

d = Distance between the plates of the capacitance.

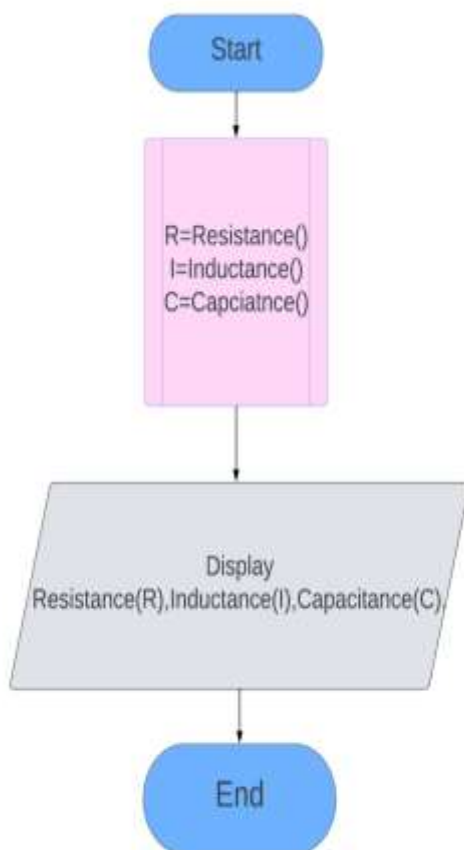


Figure 1: Flow Chart of Main Program

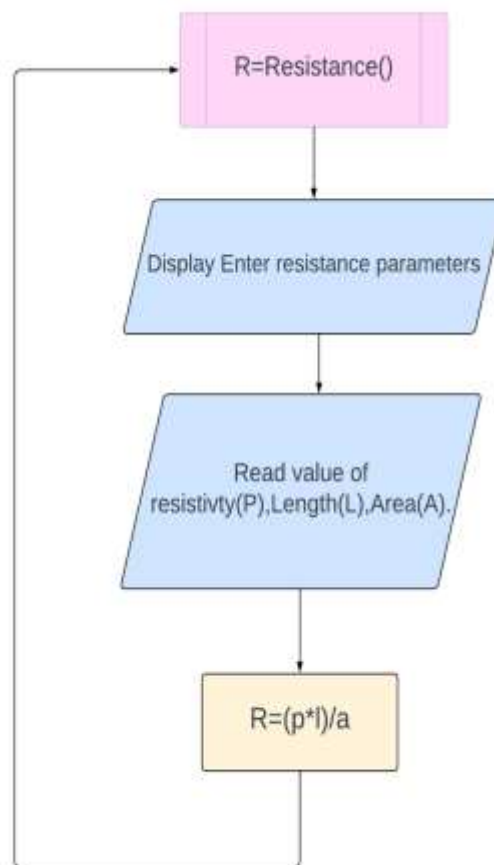


Figure 2: Flow Chart for Resistance Calculation

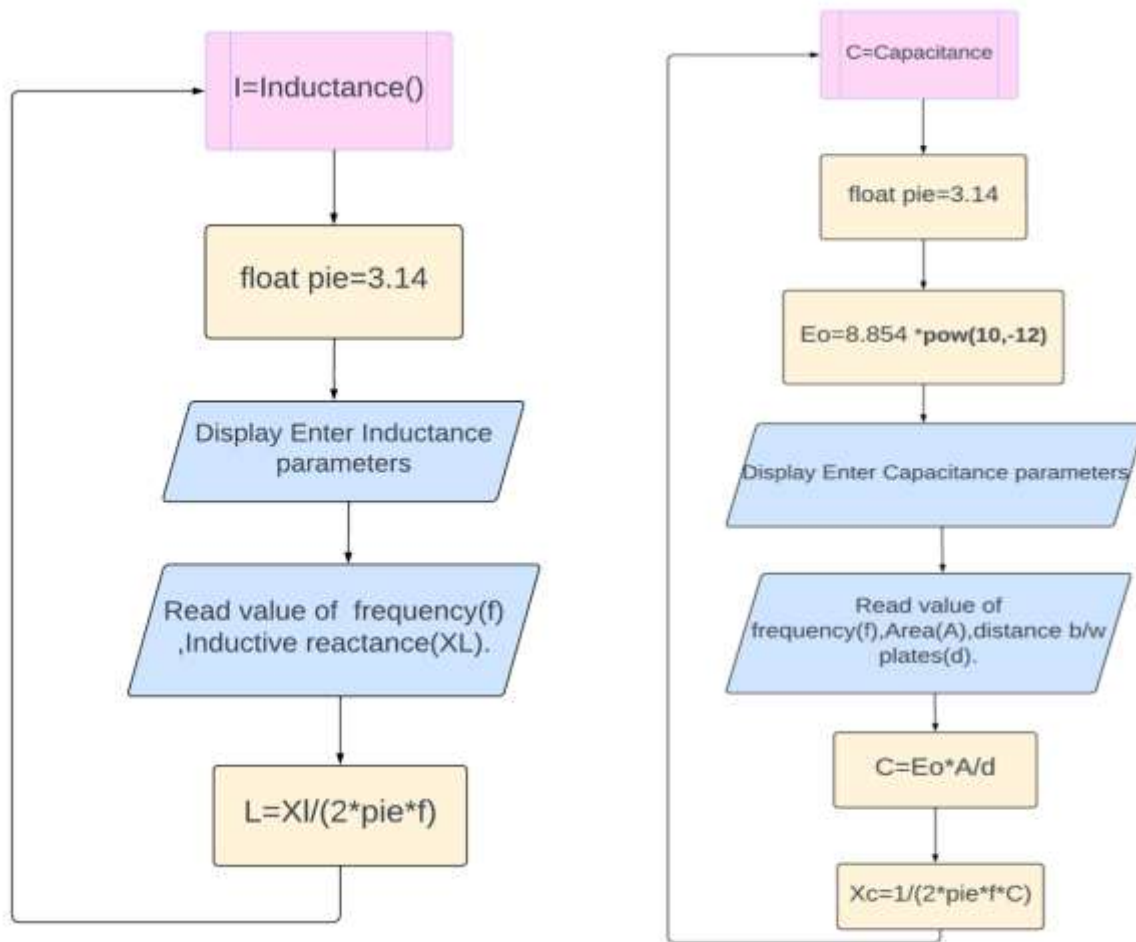


Figure 3: Flow Chart for Inductance Calculation

Figure 4: Flow Chart for Capacitance Calculation

From figure 1 the main function calls the resistance function then resistivity(ρ), area(A), length(l) are given as input values and resistance(R) is calculated (From figure 2) and Resistance value is passed to the main function. From figure 1 the main function calls the Inductance function then frequency(f), inductive reactance(XL) are given as input values and Inductance(L) is calculated (from figure 3) and inductance value is passed to the main function. From figure 1 the main function calls the Capacitance function then frequency(f), area between the plates(A), distance between the plates(d) are given as input parameters and Capacitance(C) is calculated (from figure 4) and Capacitance(C) value is passed to the main function. After all the function are called and function return the values to the main then the Resistance(R), Inductance(L), Capacitance(C) values are displayed.

RESULTS

From figure 5 with a resistivity (ρ) of 100 and a length (l) of 20, yields a relatively low resistance of 66 ohms. Inductance of approximately 1 Henry, resulting from an inductive reactance (XL) of 500 ohms at a frequency (f) of 50 Hz. The capacitance measures around 8.000000×10^{-12} farads, influenced by a moderate area of plates (30) and a distance between plates (30). From Figure 6 characterized by a higher resistivity of 200 and a longer length of 250, produces a significantly higher resistance of 1666 ohms. Inductance of approximately 2 Henry, reflecting an inductive reactance of 700 ohms at the same frequency of 50 Hz. The capacitance, at around $796.000000 \times 10^{-12}$ farads, is affected by a greater plate area (450) and a reduced distance between plates (5).

```

Enter resistor parameters:
Enter value of rho: 100
Enter length l : 20
Enter area A : 30
Enter Inductor parameters:
Enter frequency f : 50
Enter Xl : 500
Enter capacitor Parameters:
Enter frequency : 50
Enter area of plates : 30
Enter distance between plates: 30
Resistance = 66.000000 ohm's
Inductance =1.000000 Henry
Capacitance =8.000000*10^-12 farad

```

Figure 5: Values of R,L,C

```

Enter resistor parameters:
Enter value of rho: 200
Enter length l : 210
Enter area A : 30
Enter Inductor parameters:
Enter frequency f : 50
Enter Xl : 3.142
Enter capacitor Parameters:
Enter frequency : 50
Enter area of plates : 40
Enter distance between plates: 5
Resistance = 1400.000000 ohm's
Inductance =0.000000 Henry
Capacitance =70.000000*10^-12 farad

```

Figure 6: Values of R,L,C.

CONCLUSION AND FUTURE SCOPE

The aim is to find about the Resistance & Inductance & Capacitance for the given parameters by systematically analyzing capacitive reactance(X_c), resistivity(ρ), area(A). Understanding this principles is essential for designing and analyzing circuits in various application including power systems, communication systems and electronic devices. By grasping this concepts ,one can effectively analyze, design and trouble shoot electrical circuits with resistive, inductive and capacitive elements.

Resistors dissipate energy in the form of heat when current flows through them, which can lead to energy loss and reduced efficiency in some applications. The resistance of some types of resistors can vary with temperature, leading to changes in circuit performance and accuracy in temperature-sensitive applications. Resistors have tolerance ratings that specify their deviation from the nominal resistance value, which can introduce inaccuracies in circuits that require precise resistance values. Capacitors may exhibit variations in capacitance with changes in applied voltage, which can affect circuit behavior, especially in high-voltage applications. Capacitors can have leakage currents that gradually discharge the stored charge, limiting their effectiveness in applications requiring long-term energy storage. Some capacitors exhibit dielectric absorption, where a small portion of the charge remains trapped in the dielectric material after discharge, affecting their performance in certain applications. Inductors can saturate at high currents or in the presence of strong magnetic fields, causing a loss of inductance and affecting circuit performance. Inductors, especially those with high inductance values, can be bulky and heavy, making them impractical for some miniaturized or weight-sensitive

applications. Inductors can exhibit parasitic effects such as resistance and capacitance, which can introduce unwanted impedance and affect circuit behavior, especially at high frequencies.

REFERENCES

- [1]. "Electronic Principles" by Albert Melvin and David Bates
- [2]. "Engineering Circuit Analysis" by William H. Hayt Jr. and Jack E. Kemmerly
- [3]. "Introduction to Electrodynamics" by David J. Griffiths
- [4]. "Microelectronic Circuits" by Adel S. Sedra and Kenneth C. Smith .
- [5]. "Electromagnetic Field Theory Fundamentals" by Bhag Singh Guru and Hüseyin R. Hiziroglu .
- [6]. Atangana, Abdon, and Badr Saad T. Alkahtani. "Extension of the resistance, inductance, capacitance electrical circuit to fractional derivative without singular kernel." *Advances in Mechanical Engineering* 7.6 (2015): 1687814015591937.
- [7]. Gao, Yunxia, Haiyan Li, and Jing Liu. "Directly writing resistor, inductor and capacitor to composite functional circuits: a super-simple way for alternative electronics." *PLoS One* 8.8 (2013): e69761.

